

# The Principles of Operation and Applications of a 555 IC Timer



Figure 1 - Signetics 555 timer [1]

# Background

- ▣ The 555 timer is an Integrated Circuit (I.C.) containing over 40 discrete components
- ▣ It was first manufactured in 1972
- ▣ Why study such an old device?
- ▣ Designed as a universal timer: can be configured for many purposes
- ▣ Current production of over one billion devices annually!

# Terms / Abbreviations

## Concepts / terms used with the 555 timer

- ▣  $\tau$  (time constant) =  $R \times C$
- ▣ Duty Cycle (Time on / Total Time)


- ▣ Monostable
- ▣ Bistable
- ▣ Astable

New Terms

# Terms / Abbreviations

**Monostable** - one stable state (usually off)


Also called a “One Shot”

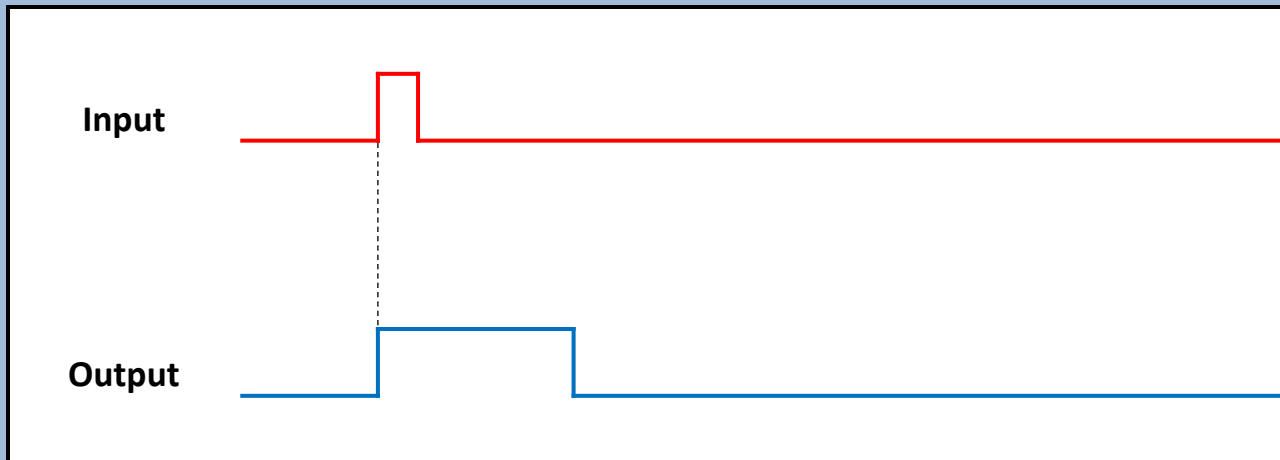

# Terms / Abbreviations

**Bistable** - Two stable states (off / on)


Also called a “Flip-Flop”

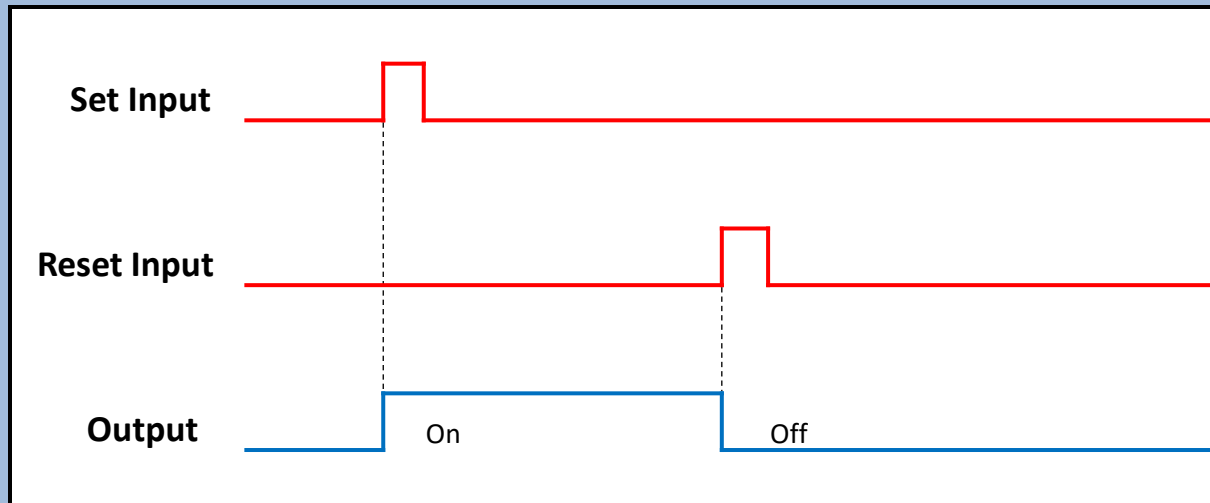
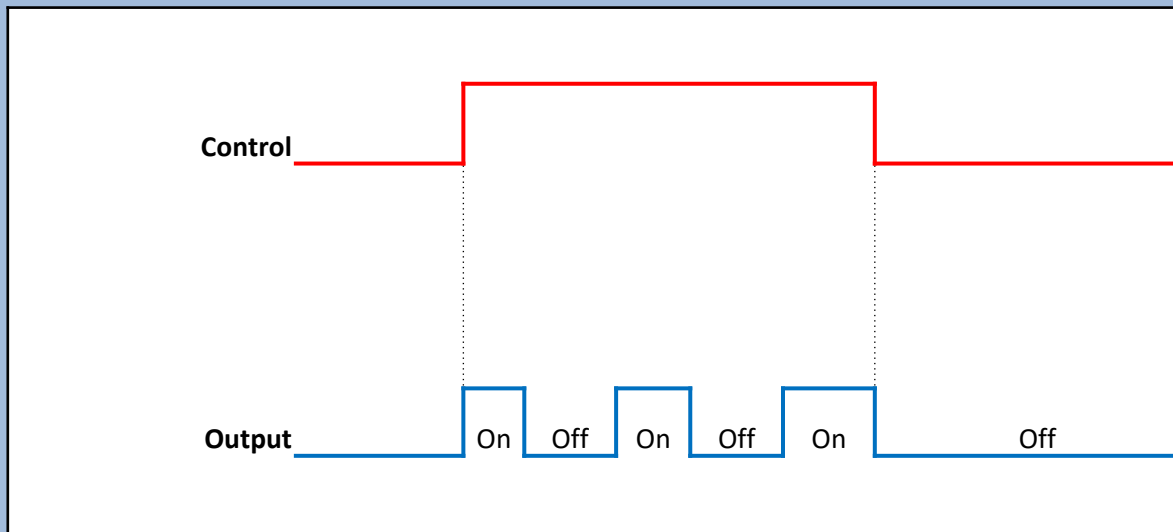
# Terms / Abbreviations


**Astable** - No stable state

- ▣ Also called an *oscillator*
- ▣ Most common application of the 555 timer



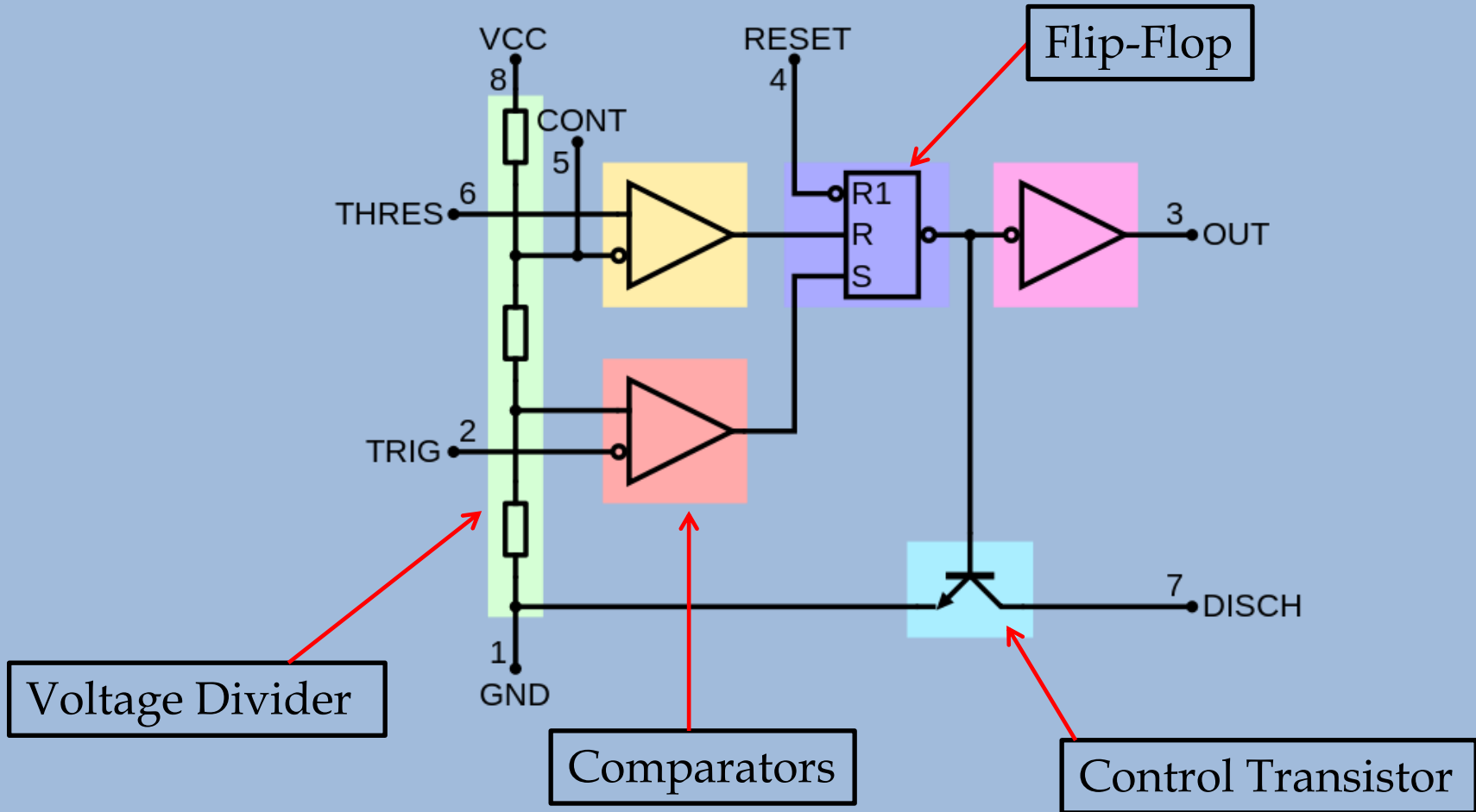
# Principles of Operation

- The 555 timer is composed of several subsystems:



# Principles of Operation

## ▣ Voltage divider:

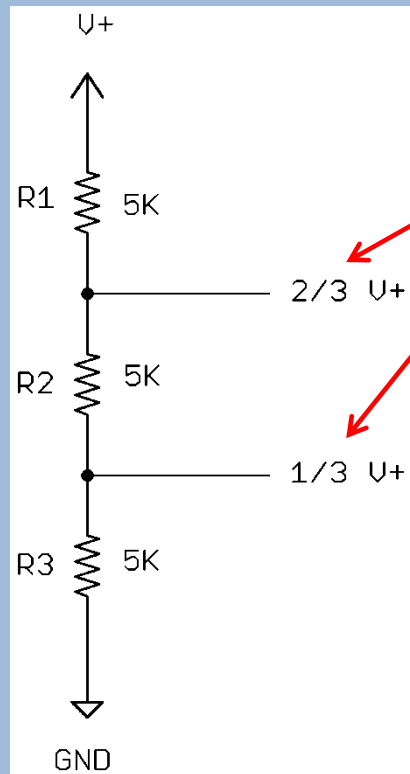


Creates two fixed voltages as percentage of total voltage



# Principles of Operation

## ▣ Comparators:

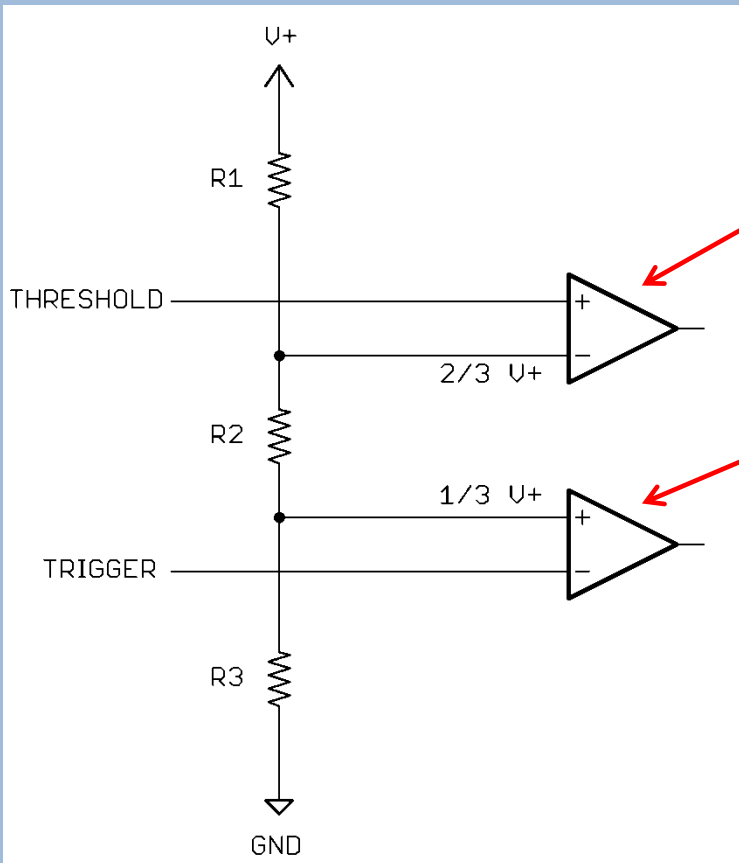

Comparator turns on output if  
voltage  $> 2/3 V+$

Comparator turns on output if  
voltage  $< 1/3 V+$


# Principles of Operation

## External RC Network:

As C charges, the voltage at the threshold / trigger point increases.


Capacitor C charges through  $R_x$  and  $R_y$

$$\tau = (R_x + R_y) \times C$$

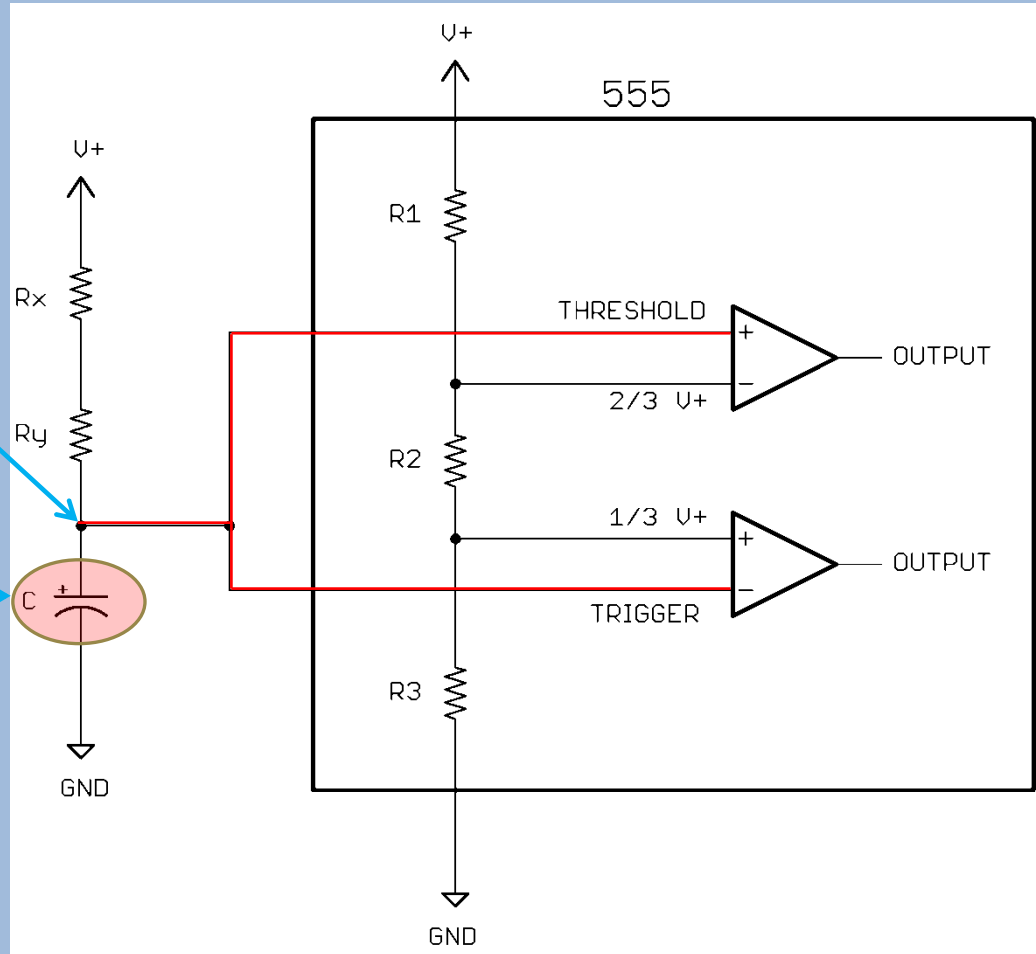


# Principles of Operation


## Flip Flop / Transistor:

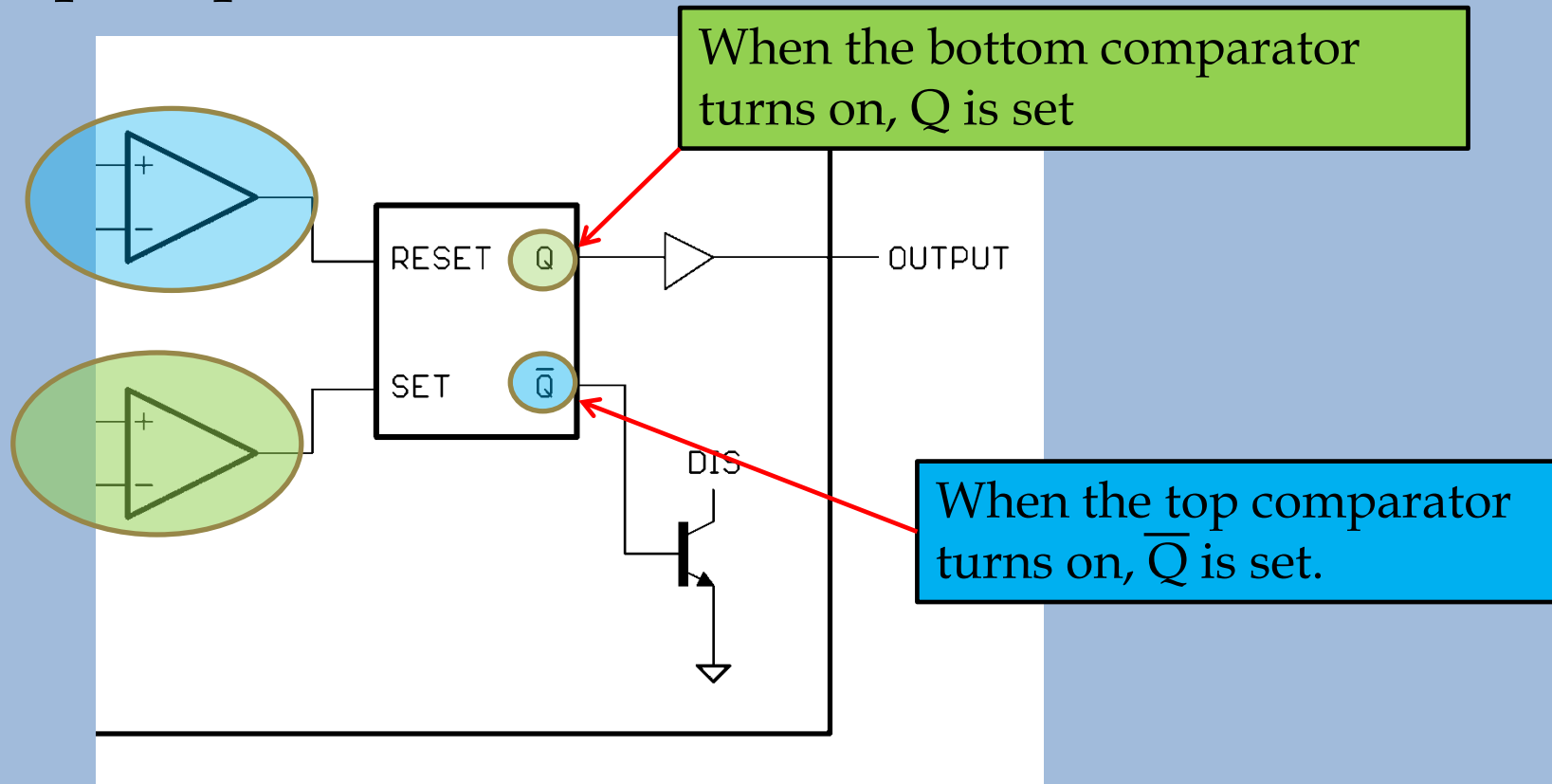

# Principles of Operation

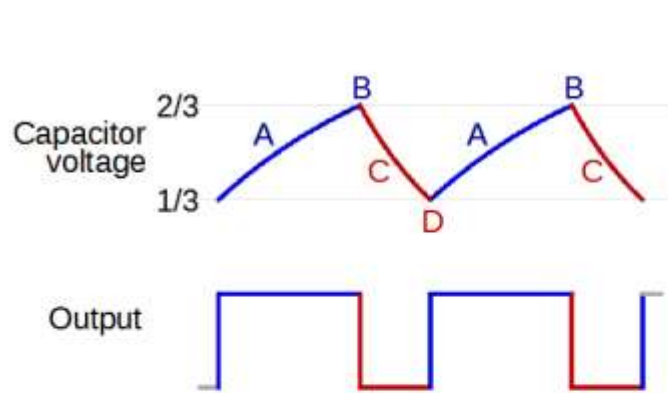


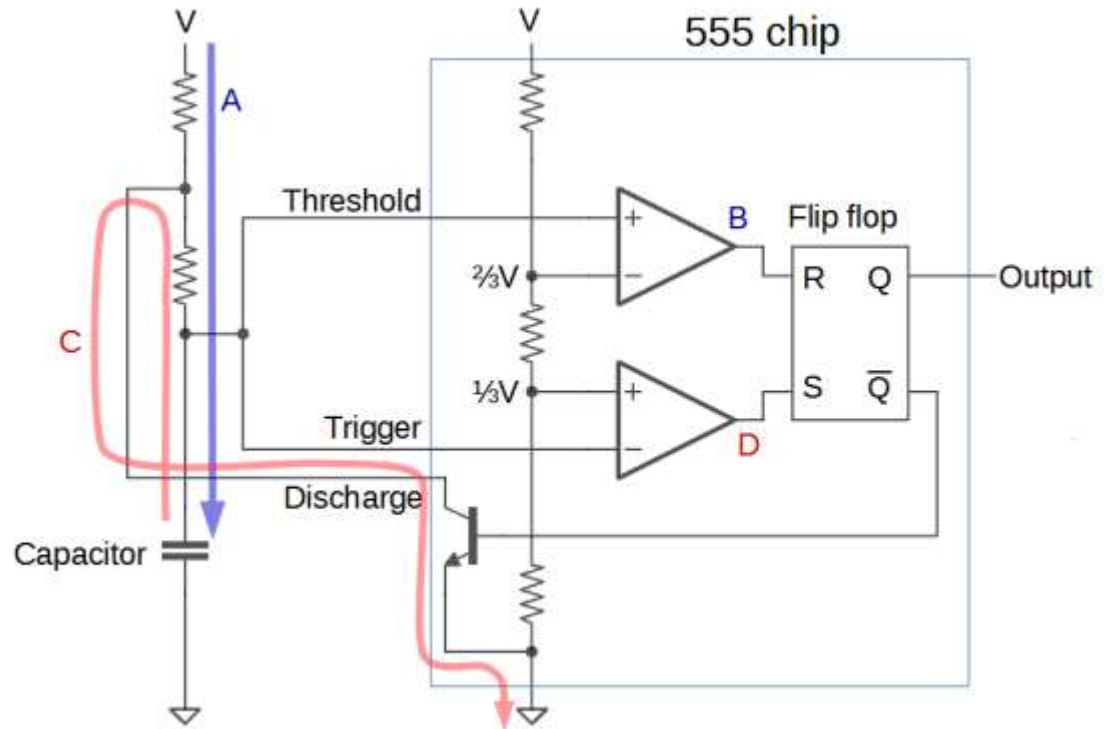- A. Capacitor charges
- B. Threshold comparator on.  
Flip flop reset.
- C. Capacitor discharges through  
discharge transistor.
- D. Trigger comparator on.  
Flip flop set.



Astable Circuit [2]

# Applications - Astable

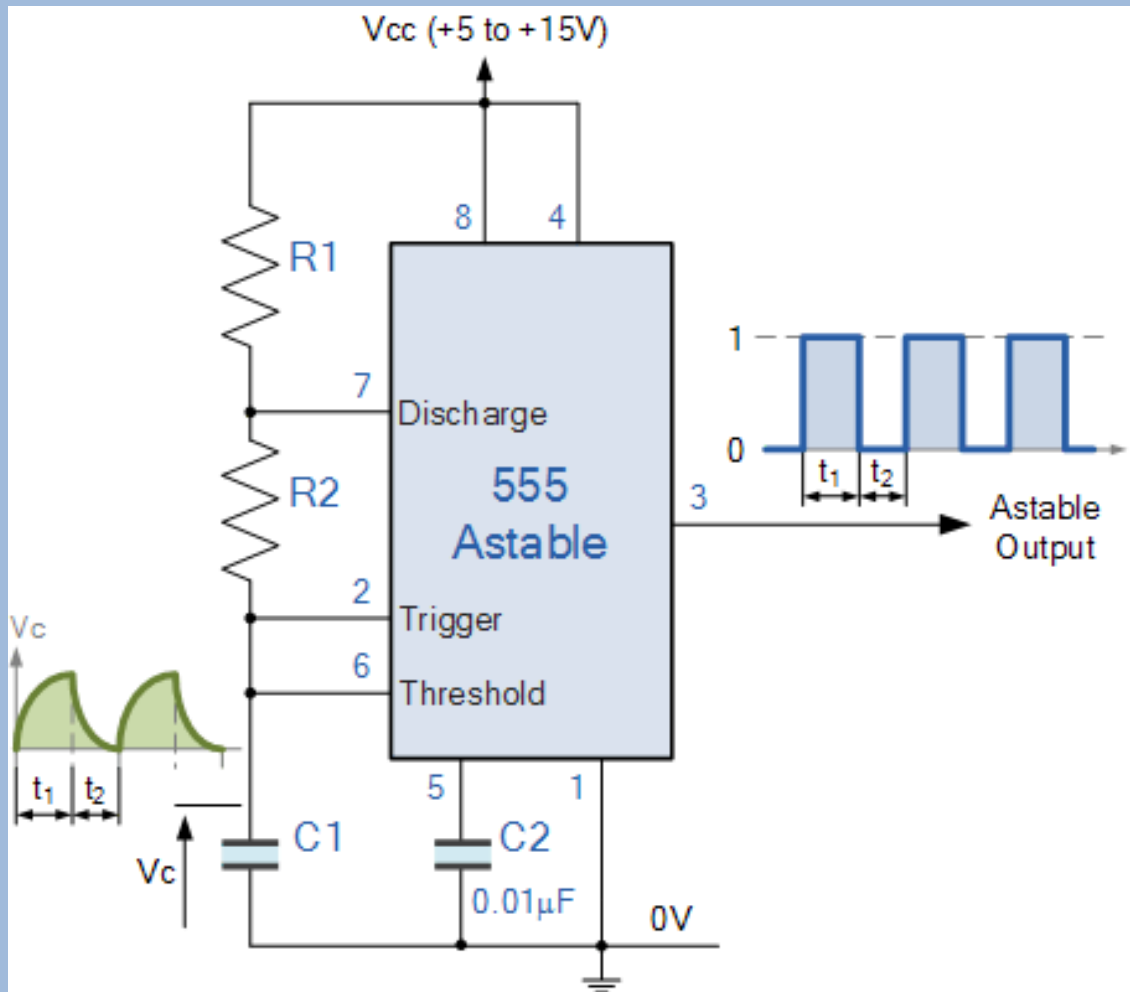

Astable Circuit [2]

# Oscillator / Timer Applications

Oscillator



Vehicle Turn Signals [3]

Oscillator  
and  
Timer



Coffee maker clock/timer [5]


Timer



Room light controller [4]
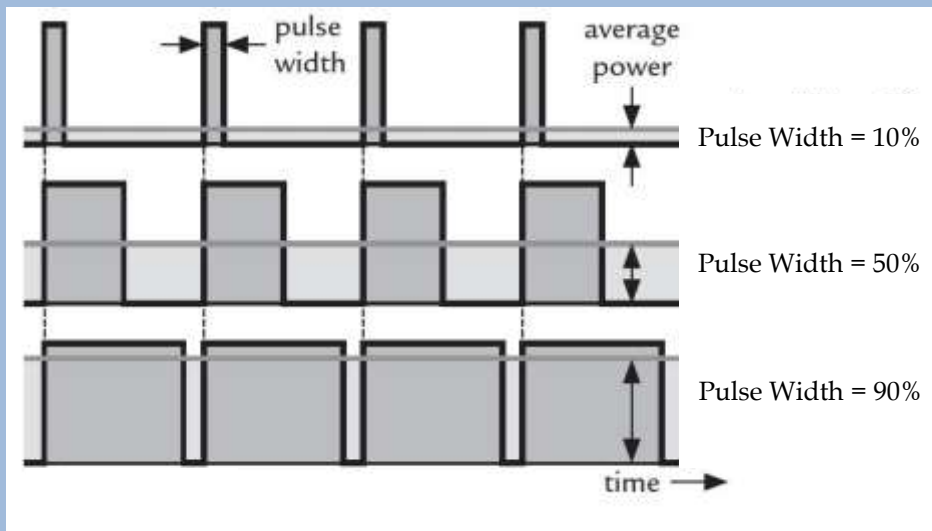
# Duty Cycle Applications

Varying the duty cycle controls the average voltage output:



Duty Cycle values [6]



Power drill speed control [7]

# Calculations required for applications:

Designing an oscillator with the 555 timer requires:

- ▣ Calculating Frequency :

$$f = \frac{1.44}{(R1+2R2) \times C}$$

- ▣ Calculating Duty Cycle :

$$DC = \frac{R1 + R2}{(R1 + 2R2)}$$



# Calculation Example

Determine the frequency and duty cycle of a 555 circuit with the following values:

$$R1 = 10.0K \quad R2 = 5.00K \quad C = 4.70\mu F$$

# In-class exercise Solution:

$$R1 = 10.0K \quad R2 = 5.00K \quad C = 4.70\mu F$$

$$f = \frac{1.44}{(10 \times 10^3 \Omega + 2 \times 5 \times 10^3 \Omega) \times 4.7 \times 10^{-6} F} = 15.4 \text{ Hz}$$

$$DC = \frac{R1 + R2}{R1 + 2R2} = \frac{10K\Omega + 5K\Omega}{(10K\Omega + 2 \times 5K\Omega)} = 75.0\%$$

# References

- ▣ 1: [http://static.righo.com/images/555/555\\_operation.png](http://static.righo.com/images/555/555_operation.png)
- ▣ 2: [www.electronics-tutorials.ws/waveforms/555\\_timer.html](http://www.electronics-tutorials.ws/waveforms/555_timer.html)
- ▣ 3: [www.aliexpress.com/](http://www.aliexpress.com/)
- ▣ 4: [www.teambasedapproach.com/03/](http://www.teambasedapproach.com/03/)
- ▣ 5: [www.severin.com/](http://www.severin.com/)
- ▣ 6: <http://www.lightinthebox.com/>
- ▣ 7: <https://www.dewalt.com>