
555 timer Oscillators – Sensors


ELTN 130
Tom Thoen
Teacher / Student / Hobbyist / Inventor

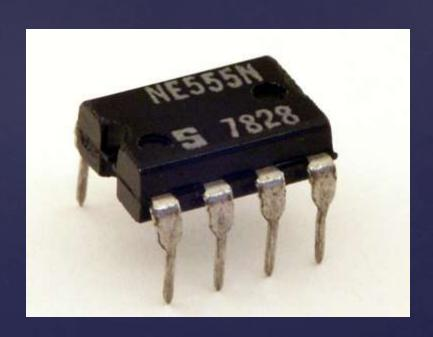
A popular IC from the past is the 555 timer. It is still used in circuits today and as of 2014 approximately 1 billion are sold each year.




What makes it so special?

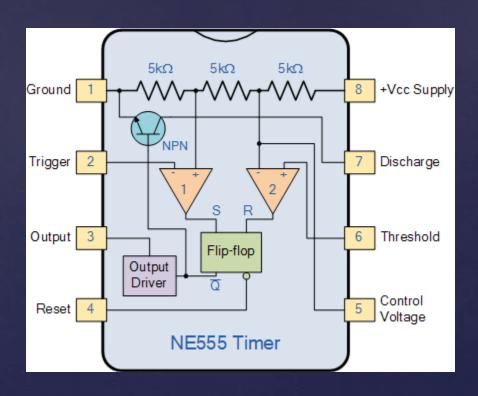
The designer created several "sub-systems" on the chip so that it can be configured to create many different types of circuits.



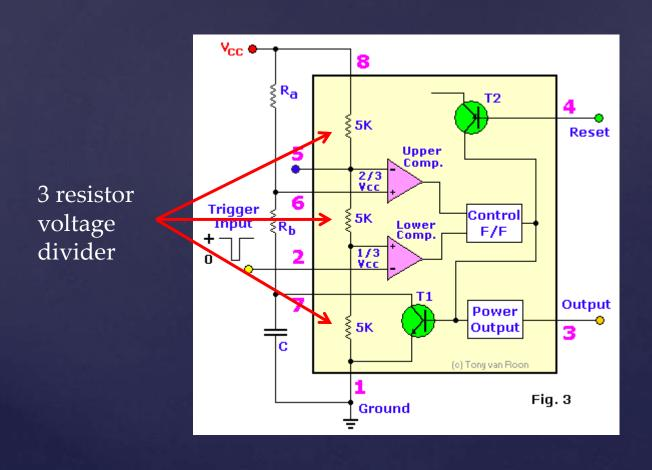


Upper and lower voltage comparators

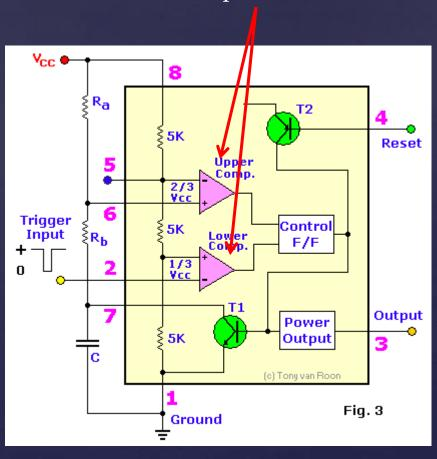


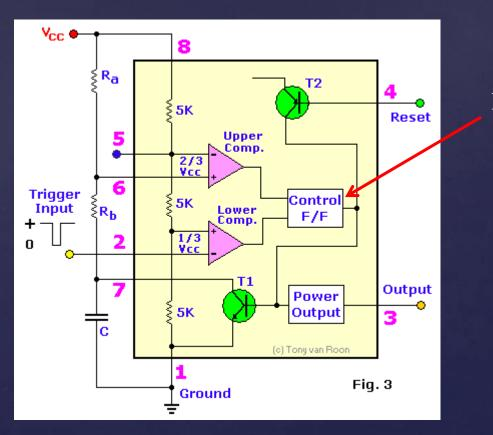


Flip - Flop

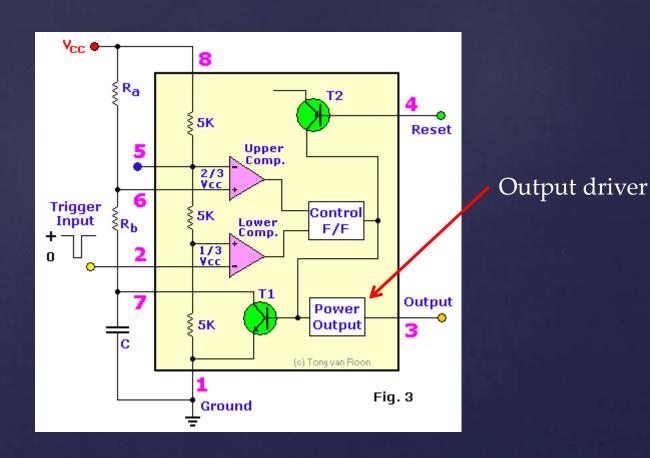

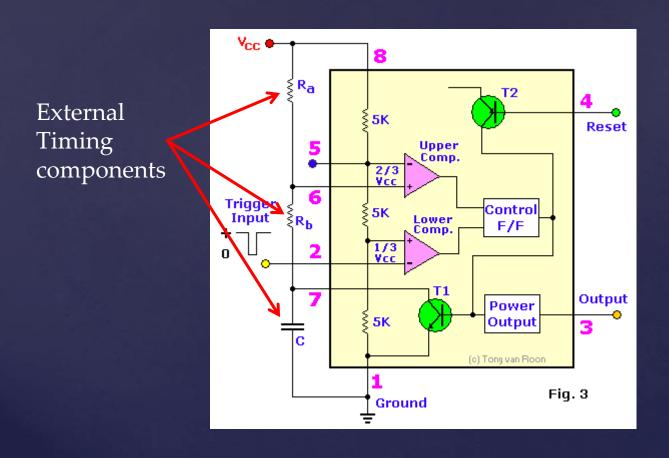
By adding just three external components (2 resistors and a capacitor) we can create many different circuits:




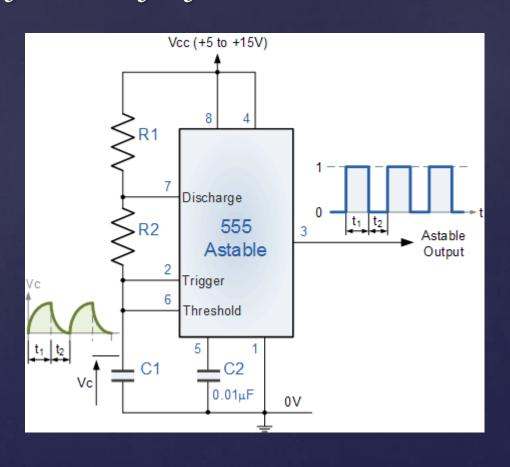An *oscillator* is a device that can produce a series of pules (think 1's and 0's) at a specific *frequency* or *duty cycle*:





Duty cycle = time on / period

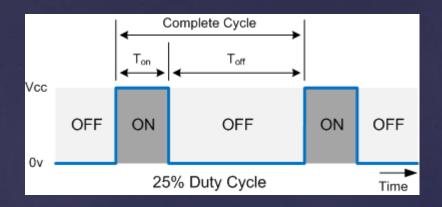

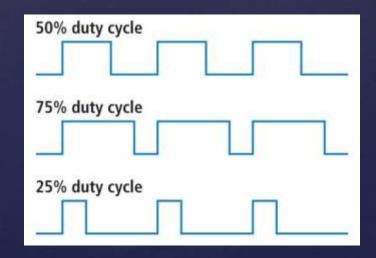

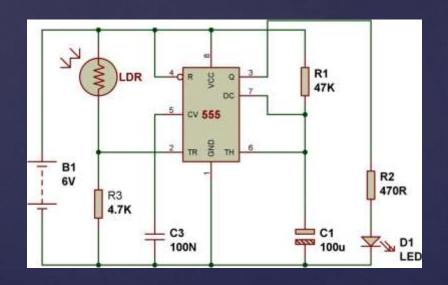We can also connect sensors to the input to control the output frequency. Also, since the output is a series of pulses, we can flash LED's or even create tones on a speaker:



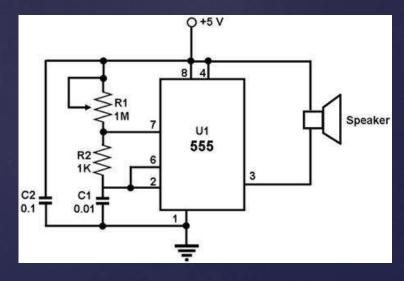

References

- www.allaboutcircuits.com
- & <u>www.wired.com</u>
- k www.pcworld.com
- k <u>www.magni.com</u>
- & <u>www.schoolphysics.co.uk</u>
- k www.pcguide.com
- 🔈 <u>www.physics.byu.edu</u>
- & www.michaelsharris.com
- & www.hamradioschool.com
- & <u>www.calctool.org</u>
- & electriciantraining.tpub.com
- & www.tandyelectronics.com
- k www.wikipdia.org
- **www.electronics-tutorials.w**s
- & <u>www.circuitstoday.com</u>