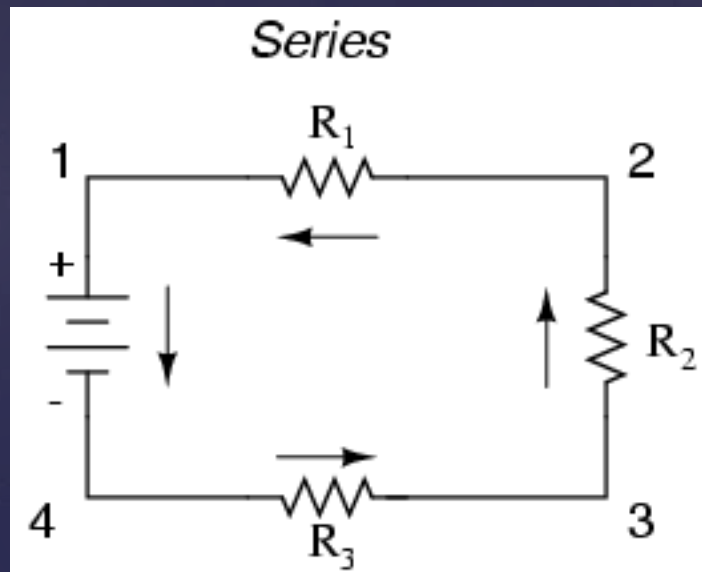


Series Circuits

{ ELTN 130
{ Tom Thoen – Teacher / Student / Hobbyist / Inventor


Resistors – how they work when connected together...

Resistors can be connected together in two basic ways: *Series* and *Parallel*.





In *Series circuits* each of the resistors are connected end to end.

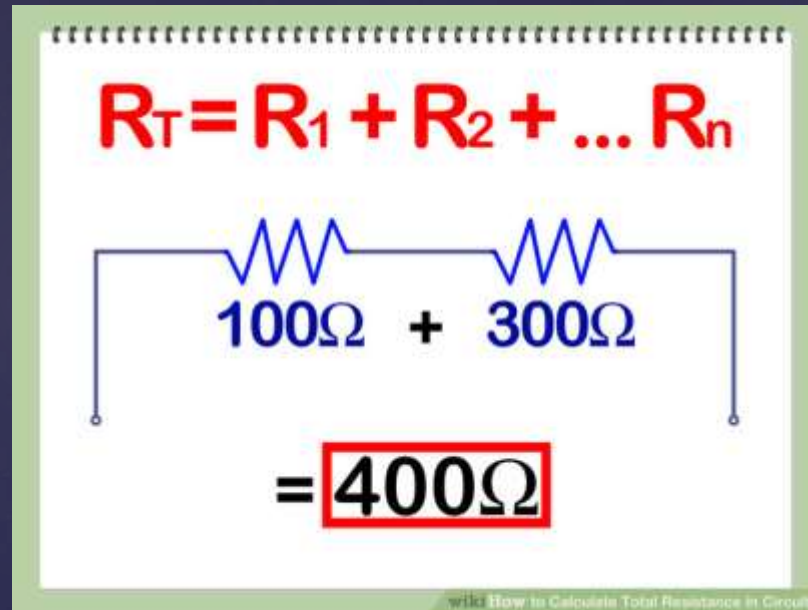Formulas for Series and Parallel resistors:



R_T = "Total Resistance" = $R_1 + R_2 + R_3 \dots$ for however many resistors there are in the circuit.

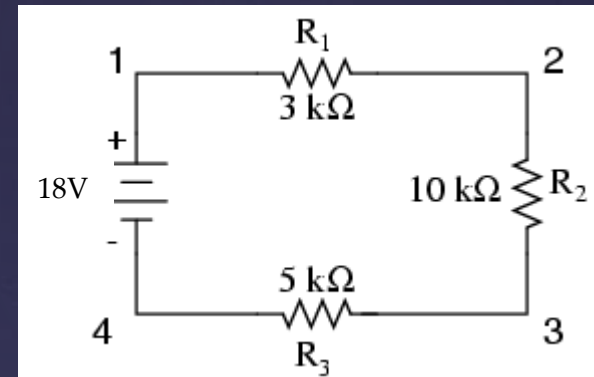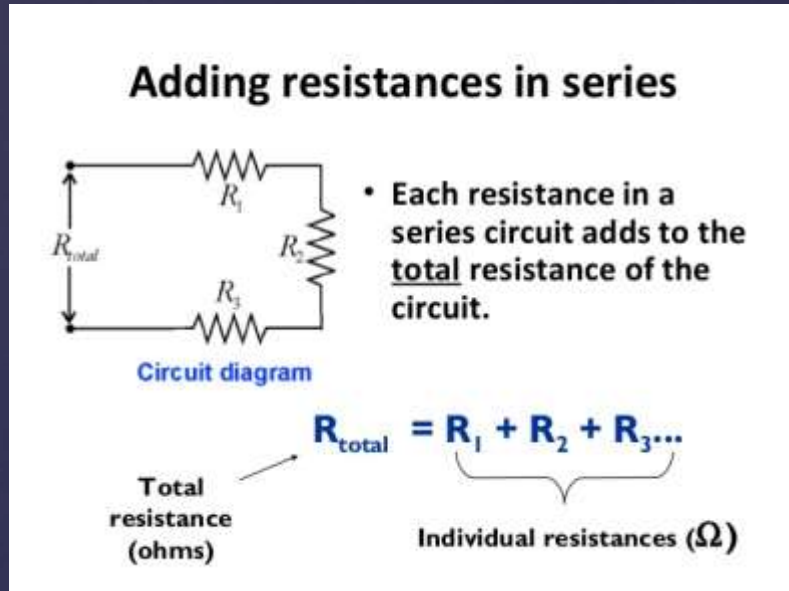To solve series circuits with more than one resistor, we start by finding the total Resistance R_T (Total Resistance).




In this example, $R_T = 3K\Omega + 10K\Omega + 5K\Omega = 18K\Omega$

Start by adding all of the resistor values together. This equals R_T


Next, we use Ohm's Law to calculate total current. This current is called I_S , or the *Source current*:

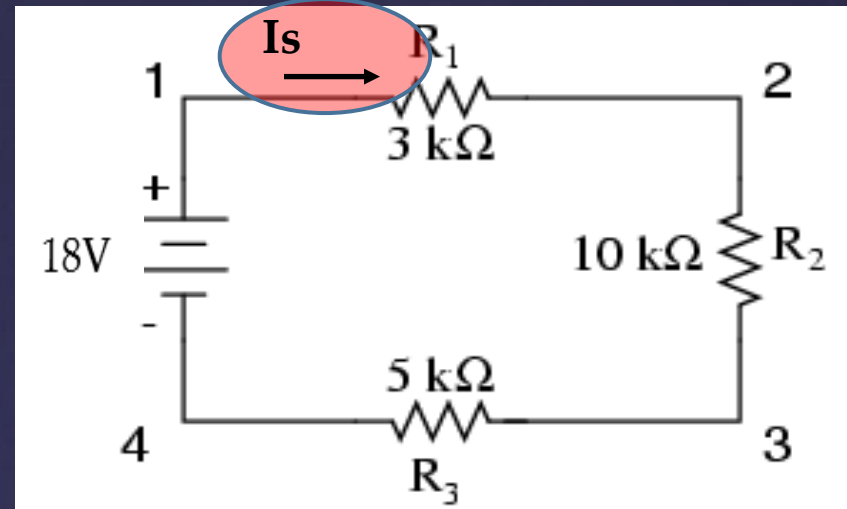1. $R_T = 18K\Omega$
2. $I_S = V/R_T$ (Ohm's Law)
3. $I_S = 18V / 18K\Omega$
4. $I_S = 0.001A$ or $1mA$




What's left? We still need to calculate the voltage across each resistor – how do we do that? Let's use Ohm's Law again...

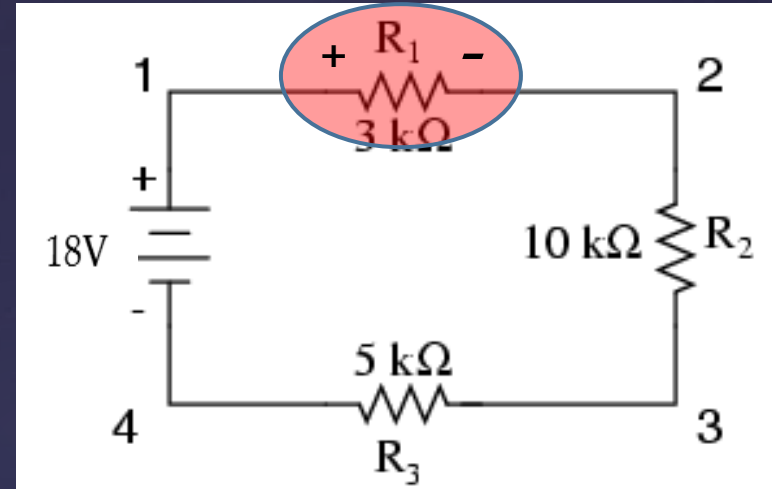1. $V_{R1} = I_S \times R1$
2. $V_{R1} = 0.001A \times 3000 \Omega$
3. $V_{R1} = 3V$




Next we calculate V_{R2} :

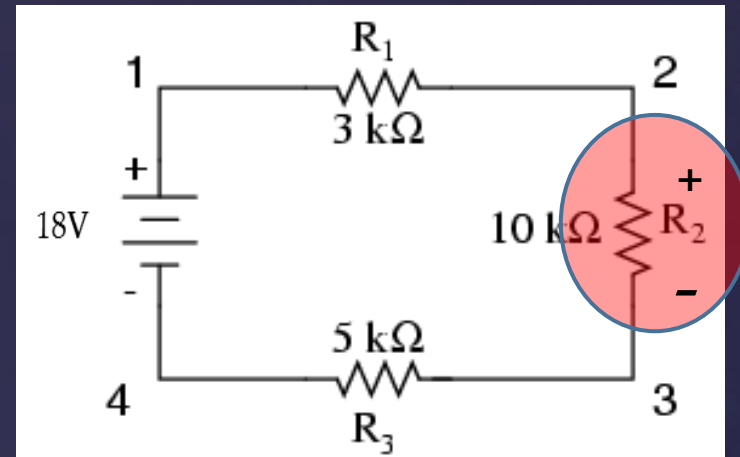1. $V_{R2} = I_S \times R2$
2. $V_{R1} = 0.001A \times 10K \Omega$
3. $V_{R1} = 10V$



Finally we calculate V_{R3} :

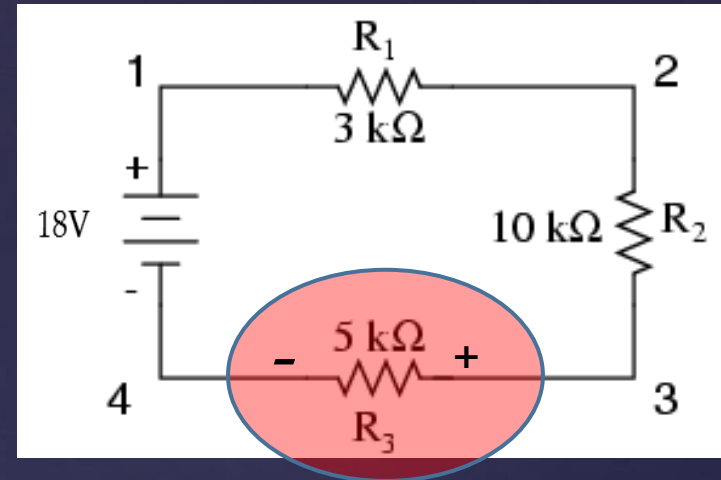1. $V_{R3} = I_S \times R3$
2. $V_{R1} = 0.001A \times 5K \Omega$
3. $V_{R1} = 5V$




Do the voltages add up?

$$V_{R1} = 3V$$

$$V_{R2} = 10V$$

$$V_{R3} = 5V$$
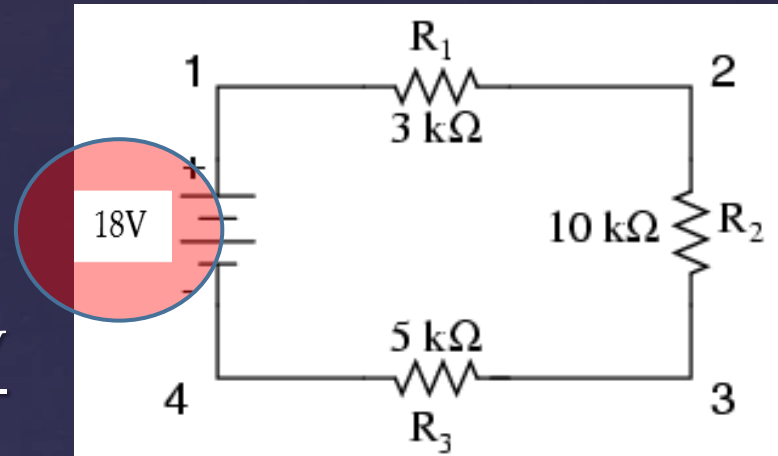
$$V_T = 3V + 10V + 5V = \underline{18V}$$



Since this matches the source voltage, we have validated that the input voltage equals the sum of the voltages across all of the resistors