

ELTN 115

UNIT 13 Capacitors

T. Thoen

Pasadena City College
School of Engineering & Technology

Capacitors – what are they?

- Capacitors are passive devices – they cannot provide “gain” in a circuit.
- Capacitors have 2 leads or wires
- Capacitors are either “non polarized” or “polarized” Polarized mean they have +/- terminals.

Capacitors – applications

- Capacitors can store energy for short periods of time.
- Capacitors can filter AC or “noisy” signals
- Capacitors can be used for timing circuits.

Packages


- Capacitors come in a variety of packages:



Electrolytic
(polarized)



Polyester
(Non-polarized)


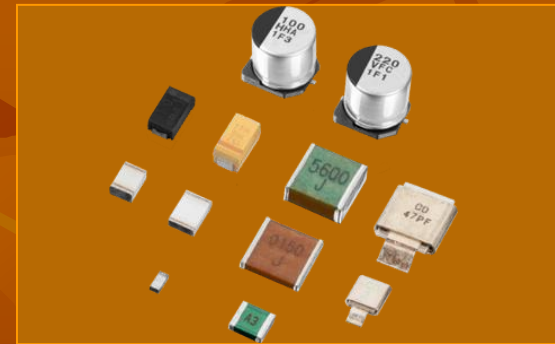


Surface Mount

Note – SMT Capacitors typically do NOT have numbers / values, except for polarized types (positive and negative leads)

Capacitors - Internal construction

What is a capacitor made of?

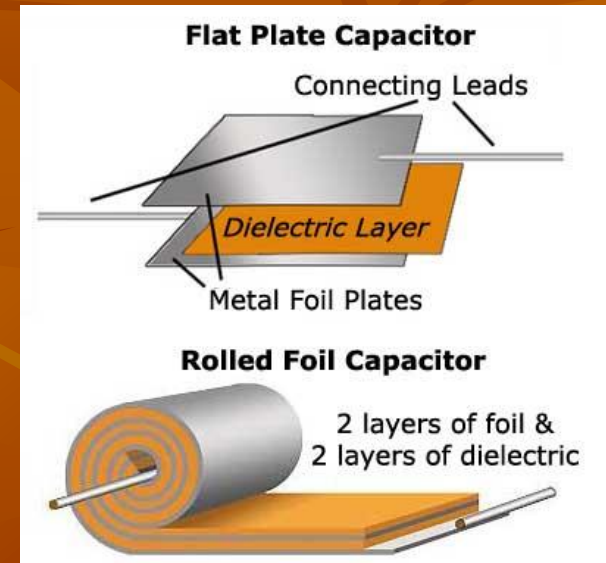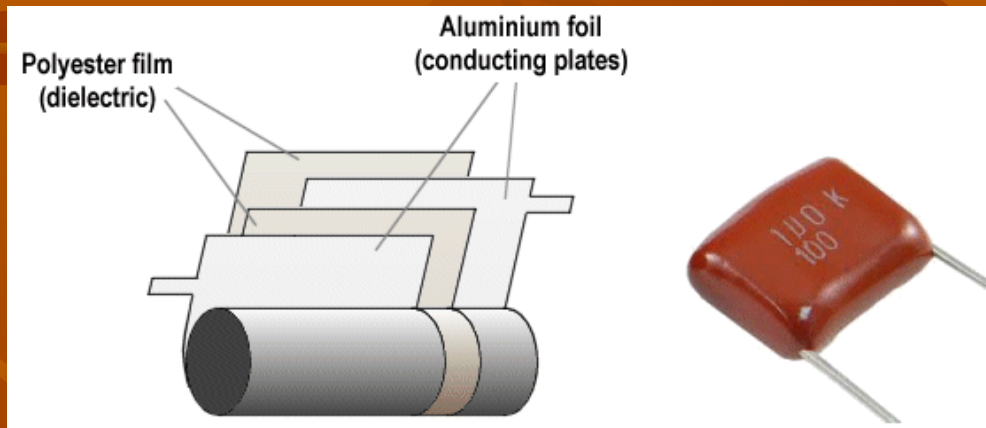

- Layers of conductors and Insulators
- Insulators are called *dielectric*
- The dielectric affects the sensitivity to temperature and other effects. There are LOTS of different types of dielectrics, often plastics are used.

Capacitor values

- Some small capacitor values are listed with numbers, not a color code: In this example, the number 104 is equal to 1×10^4 picofarads, which translates to $0.1\mu\text{F}$.



- Larger Electrolytic (polarized) capacitors have value printed on the case - This example shows $120\mu\text{F}$, 400V




Power storage:


Capacitors can charge up to a value equal to the source voltage and store the charge for a period of time.



Polarized
Capacitor


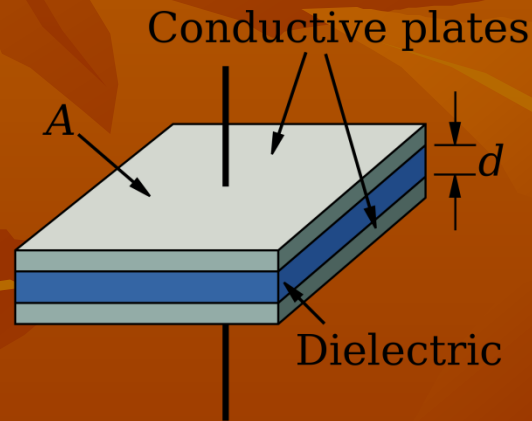


Physical
construction

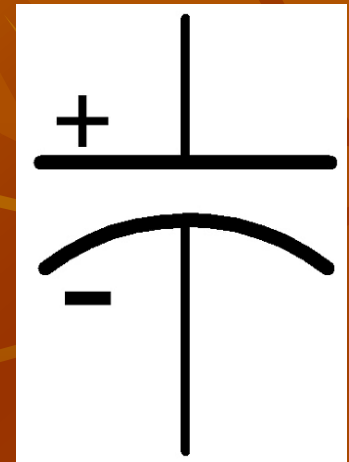



Schematic
Symbol

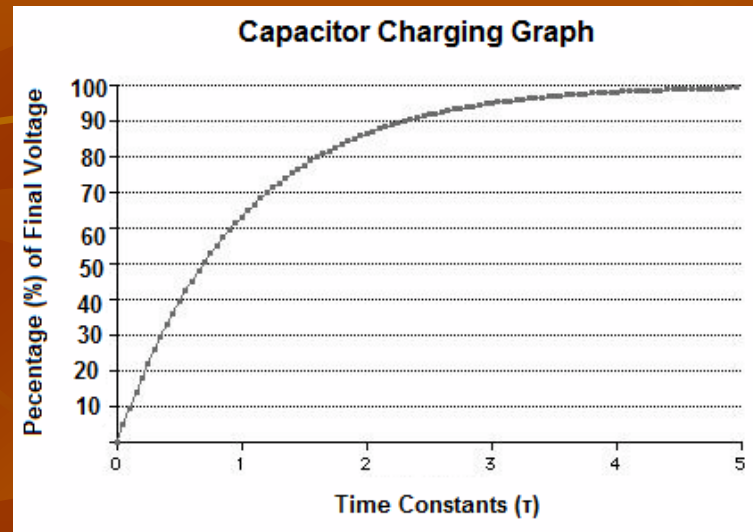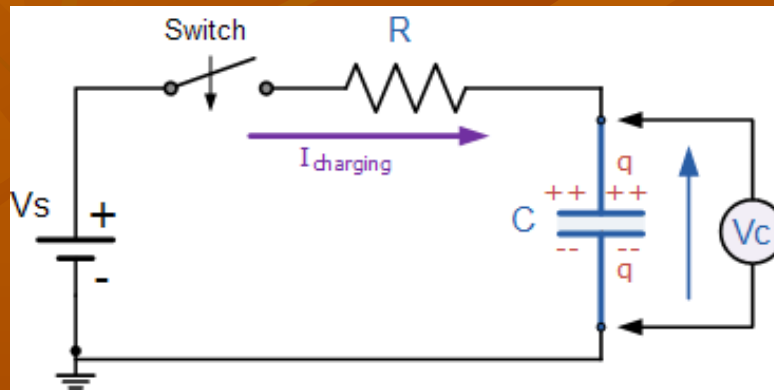When a voltage is applied across a capacitor it charges exponentially:



The rate that a capacitor charges is called tau (τ), and equals the product of the capacitor value and resistor value:

$$\tau = R \times C$$

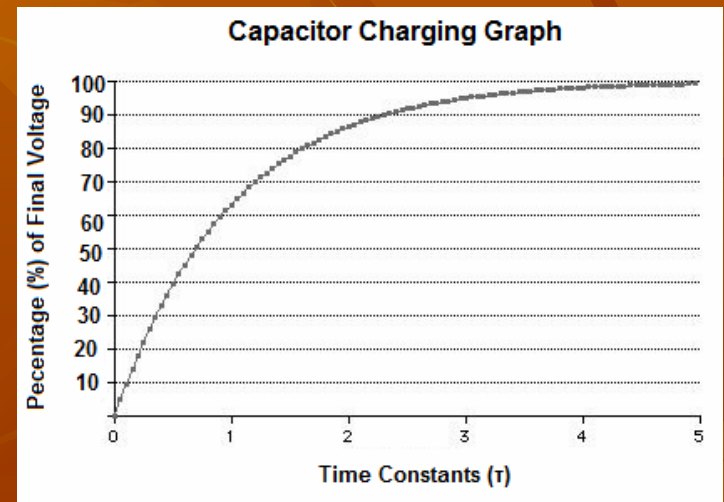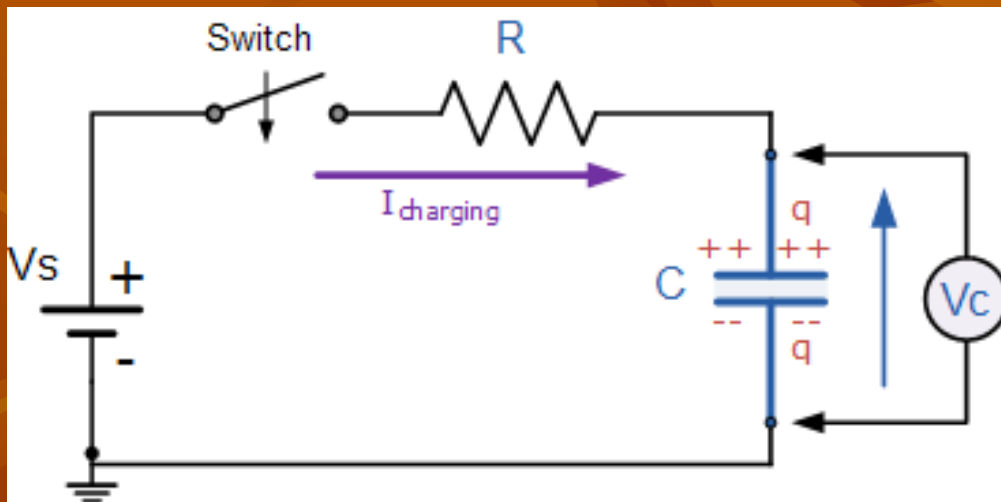

The units of tau are seconds.


- For many circuits tau has a value in milliseconds.
- A capacitor charges to the source voltage in approximately 5 time constants, or 5τ . For example:

$$\tau = R \times C$$

If $R = 1\text{K}\Omega$ and $C = 50\mu\text{F}$,

$R \times C = (1\text{K}\Omega) \times (50 \times 10^{-6} \mu\text{F}) = 50$ millisecond

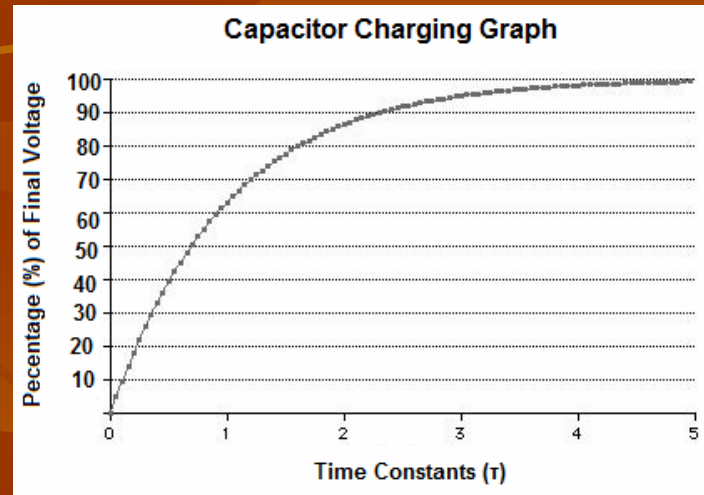So, in 250 milliseconds (1/4 second), the capacitor is fully charged.



Filtering application

- Because capacitors take time to charge, they “resist” changes in voltage.
- If a “noisy” signal is applied across a capacitor, it doesn’t have time to charge to the maximum value, so it “flattens” the output voltage:

